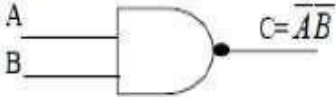
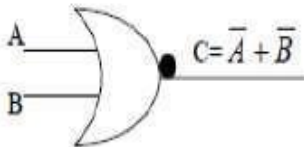
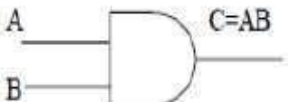
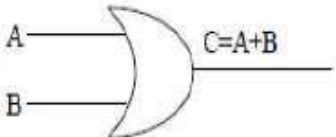
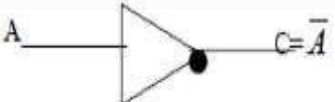
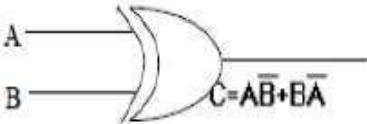


**PRACTICAL COMPONENT OF IPCC**

<b>Sl.N O</b>	<b>Experiments</b>
	<b>Simulation packages preferred: Multisim, Modelsim, PSpice or any other relevant</b>
1	Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.
2	Design a 4 bit full adder and subtractor and simulate the same using basic gates.
3	Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.
4	Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.
5	Design Verilog HDL to implement Decimal adder.
6	Design Verilog program to implement Different types of multiplexer like 2:1, 4:1 and 8:1.
7	Design Verilog program to implement types of De-Multiplexer.
8	Design Verilog program for implementing various types of Flip-Flops such as SR, JK and D.

A logic gate performs a logical operation on one or more logic inputs and produces a single logic output. The logic normally performed is Boolean logic and is most commonly found in digital circuits.

**Truth table with symbols**

S.NO	GATE	SYMBOL	INPUTS		OUTPUT
			A	B	C
1.	NAND IC 7400		0	0	1
			0	1	1
			1	0	1
			1	1	0
2.	NOR IC 7402		0	0	1
			0	1	0
			1	0	0
			1	1	0
3.	AND IC 7408		0	0	0
			0	1	0
			1	0	0
			1	1	1
4.	OR IC 7432		0	0	0
			0	1	1
			1	0	1
			1	1	1
5.	NOT IC 7404		1	-	0
			0	-	1
6.	EX-OR IC 7486		0	0	0
			0	1	1
			1	0	1
			1	1	0

Verilog is a hardware description language (HDL) that is used to describe digital systems and circuits in the form of code. It was developed by Gateway Design Automation in the mid-1980s and later acquired by Cadence Design Systems.

Verilog is widely used for design and verification of digital and mixed-signal systems, including both application-specific integrated circuits (ASICs) and field-programmable gate arrays (FPGAs). It supports a range of levels of abstraction, from structural to behavioral, and is used for both simulation-based design and synthesis-based design.

The language is used to describe digital circuits hierarchically, starting with the most basic elements such as logic gates and flip-flops and building up to more complex functional blocks and systems. It also supports a range of modeling techniques, including gate-level, RTL-level, and behavioral-level modeling.

A Verilog program can be simulated in **Xilinx** Project Navigator. Xilinx ISE (Integrated Synthesis Environment) is a discontinued software tool from Xilinx for synthesis and analysis of HDL designs, which primarily targets development of embedded firmware for Xilinx FPGA and CPLD integrated circuit (IC) product families.

#### VERILOG CODE

```
module allgate ( a, b, yand,yor,ynot,ynand,ynor,yxor,yxnor );
input a,b;
output yand, yor, ynot, ynand, ynor, yxor, yxnor;

assign yand = a&b;           // ANDOperation
assign yor = a|b;           // OROperation
assign ynot = ~a;           // NOTOperation
assign ynand = ~(a&b);      // NANDOperation
assign ynor = ~(a|b);       //NOROperation
assign yxor = a^b;          //XOROperation
assign yxnor=~(a^b);        //XNOROperation
endmodule                   // END of themodule
```

- Given a 4-variable logic expression, simplify it using appropriate technique and simulate the same using basic gates.


Design:

Consider the function  $f(a,b,c,d) = \sum m(3,7,11,12,13,14,15)$

cd \ ab	00		01		11		10	
	0	1	0	1	0	1	0	1
00	0	0	0	0	1	1	0	0
01	0	0	0	0	1	1	0	0
11	1	1	1	1	1	1	1	1
10	0	0	0	0	1	1	0	0

$$Y = ab + cd$$

Circuit Diagram

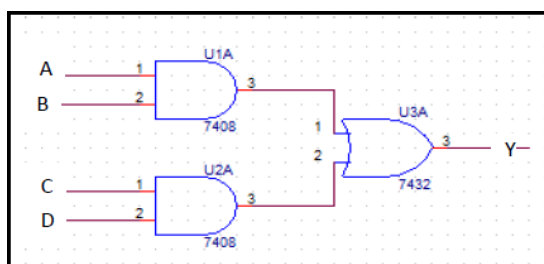


Truth Table

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

**Verilog Code**

```
module f(a,b,c,d,e);  
    Input a,b,c,d;  
    Output e;  
    Assign e=a&b | c&d;  
endmodule
```

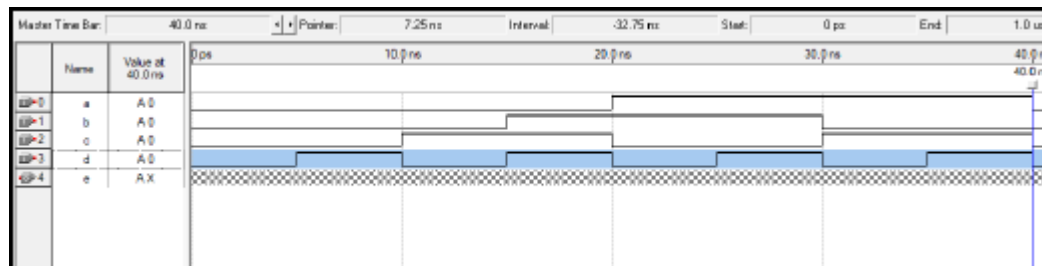**Output**

The four variable logic expression is simplified using K-map and simplified the same using basic gates.

## 2. Design a 4 bit full adder and subtractor and simulate the same using basic gates.

### Design for Full Adder


#### Truth Table

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = A'B'C + A'BC' + AB'C' + ABC$$

$$\text{Cout} = A'BC + AB'C + ABC' + ABC$$

### Circuit Diagram of 4-bit Full Adder

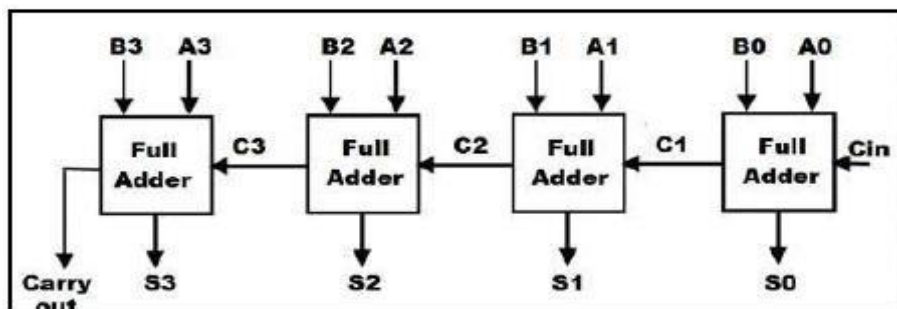

### Verilog code


```

module fa(a,b,cin,sum,cout);
    input a,b,cin;
    output sum,cout;
    assign sum = ((!a & !b & cin) | (!a & b & !c) | (a & !b & !c) | (a & b & c));
    assign cout = ((!a & b & c) | (a & !b & c) | (a & b & !c) | (a & b & c));
endmodule

module fourbitadder(a,b,sum,c);
    input [3:0]a;
    input [3:0]b;
    output [3:0]sum;
    output c;
    wire c1,c2,c3;
    fa g0(a[0],b[0],0,sum[0],c1);
    fa g1(a[1],b[1],c1,sum[1],c2);
    fa g2(a[2],b[2],c2,sum[2],c3);
    fa g3(a[3],b[3],c3,sum[3],c);
endmodule

```

## Output

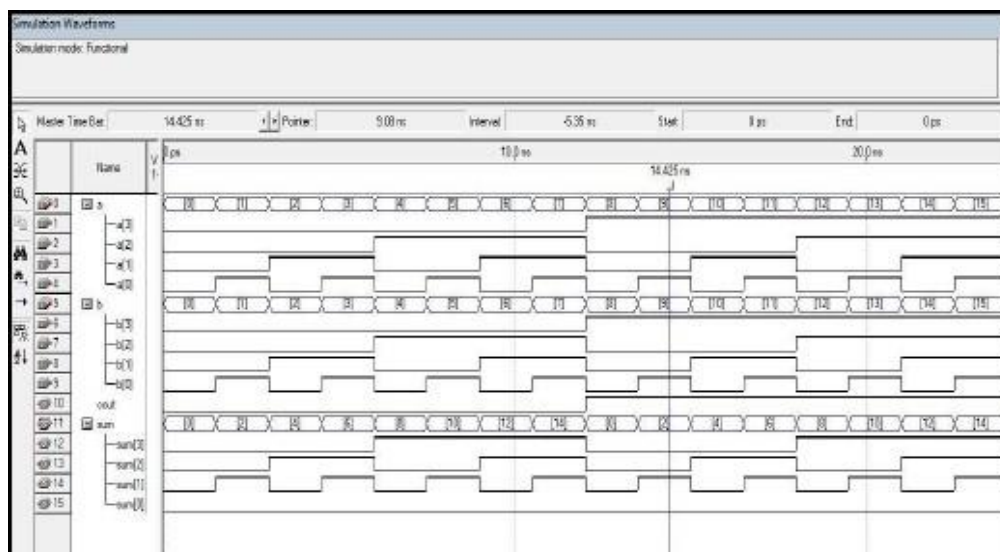

## Design for Full Subtractor


### Truth Table

A	B	Cin	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Sum} = A'B'C + A'BC' + AB'C' + ABC$$

$$\text{Cout} = A'B'C + A'BC' + A'BC + ABC$$
 
## Circuit diagram of four bit full Subtractor




## Verilog Program

```
module fs(a,b,c,d,bout);
    input a,b,c;
    output d,bout;
    assign d = ((!a&!b&c) | (!a&b&!c) | (a&!b&!c) | (a&b&c));
    assign bout = ((!a&!b&c) | (!a&b&!c) | (!a&b&c) | (a&b&c));
endmodule
```

```
module fourbitsub(a,bin,diff,bout);
    input [3:0]a;
    input [3:0]bin;
    output [3:0]diff;
    output bout;
    wire b1,b2,b3;

    fs g0(a[0],bin[3],0,diff[0],b1);
    fs g1(a[1],bin[2],b1,diff[1],b2);
    fs g2(a[2],bin[1],b2,diff[2],b3);
    fs g3(a[3],bin[0],b3,diff[3],bout);
endmodule
```

## Output

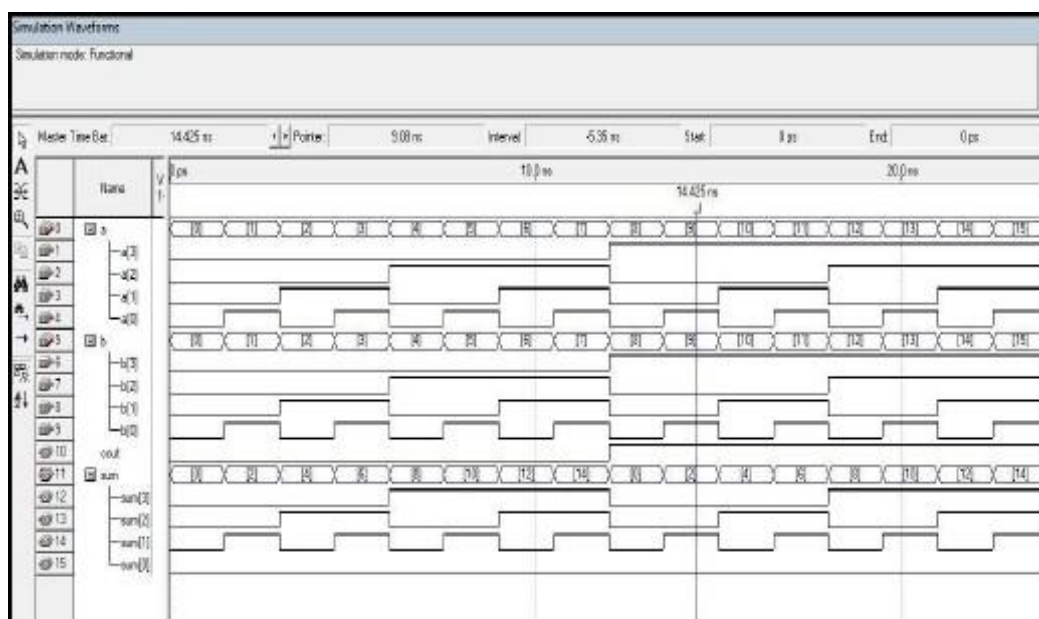

The four bit full adder and Subtractor is designed and simulated the same using basic gates.




### 3. Design Verilog HDL to implement simple circuits using structural, Data flow and Behavioural model.

#### Design of a simple OR Gate

##### Truth table

A	B	Y=A + B
0	0	0
0	1	1
1	0	1
1	1	1

 

##### Structural model

```
module structural(a,b,y);
    input a,b;
    output y;
    or g1(y,a,b);
endmodule
```

##### Dataflow model

```
module dataflow(a,b,y);
    input a,b;
    output y;
    assign y=a | b;
endmodule
```

##### Behavioural model

```
module beh(a,b,y);
    input a,b;
    output y;
    reg y;
    always @(a or b)
        begin
            if((a==0)&&(b==0))
                y=0;
            else
                y=1;
        end
endmodule
```

## Output

		40.000 ns							
Name	Value	0.000 ns	5.000 ns	10.000 ns	15.000 ns	20.000 ns	25.000 ns	30.000 ns	35.000 ns
a	1								
b	1								
y	1								

The simple OR gate is implemented using Structural, Dataflow and Behavioral model.

#### 4. Design Verilog HDL to implement Binary Adder-Subtractor – Half and Full Adder, Half and Full Subtractor.


##### Design of Half Adder

INPUTS		OUTPUTS	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = A \cdot B$$

##### Circuit Diagram

 


##### Verilog Code

```

module ha(a,b,s,c);
    input a,b;
    output s,c;
    assign s=a^b;
    assign c=a&b;
endmodule

```

##### Output

 


## Design of Full Adder

INPUTS			OUTPUTS	
A	B	C <sub>in</sub>	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C = C_{in} (A \oplus B) + AB$$

## Circuit Diagram

 


## Verilog Code

```

module fa(a,b,cin,s,cout);
    input a,b,cin;
    output s,cout;
    assign s = a^b^cin;
    assign cout=(c&(a^b))|(a&b);
endmodule

```

## Output

 


## Design of Half Subtractor

A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = \overline{A}.B + A.\overline{B}$$

$$B_0 = \overline{A}.B$$

### Circuit diagram

 


### Verilog code

```

module hs(a,b,d,bout)
    input a,b;
    output d,bout;
    assign d=a^b;
    assign bout=!a&b;
endmodule

```

### Output

 


## Design of full Subtractor

Inputs			Outputs	
A	B	Borrow <sub>in</sub>	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d = A \oplus B \oplus C$$

$$b = C(A \odot B) + \overline{A}B$$

## Circuit diagram

 


## Verilog Code

```

module fs(a,b,bin,d,bout);
    input a,b,bin;
    output d,bout;
    assign d=a^b^bin;
    assign bout=(!a&(b^bin))|(b&bin);
endmodule

```

## Output

 

The truth table of half adder, full adder, half Subtractor, and full Subtractor are verified.

### 5. Design Verilog HDL to implement Decimal adder.

#### Design

Sum bits of adder-1 →

INPUTS				OUTPUT
S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


	S <sub>1</sub> S <sub>0</sub>	00	01	11	10
S <sub>3</sub> S <sub>1</sub>	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	1

→ S<sub>3</sub>S<sub>2</sub>

→ S<sub>3</sub>S<sub>1</sub>

$$Y = S_3S_2 + S_3S_1$$

#### Circuit diagram

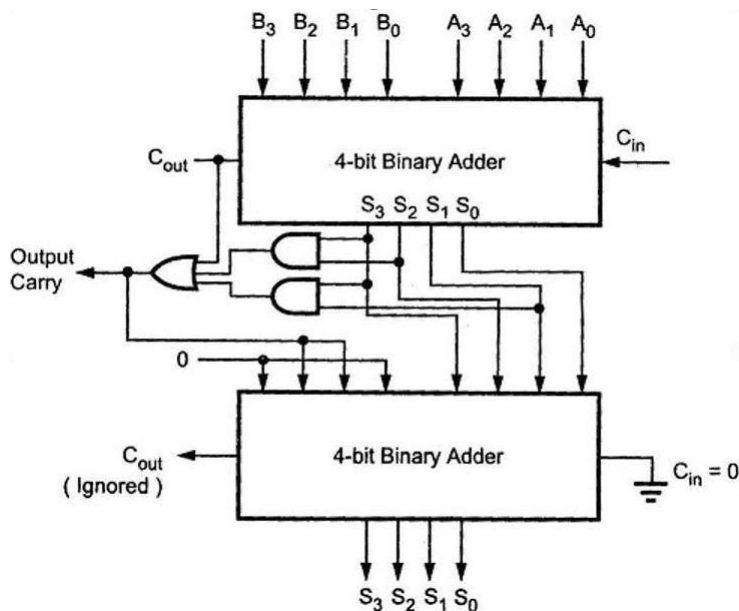

**Verilog code**

```

module bcd(a,b,carry_in,sum,carry);

//declare the inputs and outputs of the module with their sizes.
    input [3:0] a,b;

    input carry_in;
    output [3:0] sum;
    output carry;

//Internal variables

    reg [4:0] sum_temp;

    reg [3:0] sum; reg carry;

//always block for doing the addition
    always @(a,b,carry_in)
    begin

        sum_temp = a+b+carry_in; //add all the inputs
        if(sum_temp > 9)

            begin

                sum_temp = sum_temp+6; //add 6, if result is more than 9.
                carry = 1; //set the carry output

                sum = sum_temp[3:0];

            end
        else
            begin

                carry = 0;

                sum = sum_temp[3:0];

            end
    end
endmodule

```

**Output**

Name	Value	2 us	3 us	4 us
x[3:0]	0100	0110	1001	0101
y[3:0]	0111	0111	1000	0010
sum[4:0]	01011	01101	10001	00111
adjust	1			
s[4:0]	10001	10011	10111	00111


Decimal Adder is implemented using Verilog code and simulated and its functioning correctly for all possible values.



## 6. Design Verilog program to implement Different types of multiplexer like 2:1, 4:1 and 8:1.

### Design of 2:1 Multiplexer

S	Y
0	I <sub>0</sub>
1	I <sub>1</sub>

 


### Verilog code

```


module mux2_1( I, sel, y);
    input [1:0] I;
    input sel;
    output y;
    reg y;
    always@ (sel , I)
    begin
        case (sel)
            1'b0: y = I [0];
            1'b1: y = I [1];
        endcase
    end
endmodule
  
```

### Output

 

## Design of 4:1 Multiplexer

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>

 


## Verilog code

```

module mux_4_1 (I, sel, y);
    input [3:0] I;
    input [1:0] sel;
    output y;
    reg y;
    always@ (sel, I)
        begin
            case (sel)
                2'b00: y = I [0];
                2'b01: y = I [1];
                2'b10: y = I [2];
                default: y = I [3];
            endcase
        end
endmodule
end


```

## Output

 

## Design of 8:1 Multiplexer

$S_2$	$S_1$	$S_0$	$Y$
0	0	0	I <sub>0</sub>
0	0	1	I <sub>1</sub>
0	1	0	I <sub>2</sub>
0	1	1	I <sub>3</sub>
1	0	0	I <sub>4</sub>
1	0	1	I <sub>5</sub>
1	1	0	I <sub>6</sub>
1	1	1	I <sub>7</sub>

 

## Verilog code

```

module mux_8_1 (I, sel, y);
    input [7:0] I;
    input [2:0] sel;
    output y;
    reg y;
    always@ (sel, I )
        begin
            case (sel)
                3'b000: y = I [0];
                3'b001: y = I [1];
                3'b010: y = I [2];
                3'b011: y = I [3];
                3'b100: y = I [4];
                3'b101: y = I [5];
                3'b110: y = I [6];
                default: y = I [7];
            endcase
        end
endmodule
end

```


## Output



## 7. Design Verilog program to implement types of De-Multiplexer.

### Design of 1:2 Demultiplexer

Select	Input	Outputs	
S	D	Y <sub>2</sub>	Y <sub>1</sub>
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

 


### Verilog Code

```

module de_mux_1_2 (I, sel, y);
    input I;
    input sel;
    output reg [1:0] y;
    always@ (sel, I)
        begin
            case (sel)
                1'b0: begin y [0] = I; y [1] = 1'b0; end
                1'b1: begin y [0] = 1'b0 ; y [1] = I; end
            endcase
        end
endmodule


```

### Output

 

### Design of 1:4 Demultiplexer

sel[0]	sel[1]	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	0	i	0	0	0
0	1	0	i	0	0
1	0	0	0	i	0
1	1	0	0	0	i

 


### Verilog Code

```

module de_mux_1_4 (I, sel, y);
    input I;
    input [1:0] sel;
    output reg [3:0] y;
    always@ (sel, I)
        begin case (sel)
            2'b00: begin y [0] = I; y [1] = 0; y [2] = 0; y [3] = 0; end
            2'b01: begin y [0] = 0; y [1] = I; y [2] = 0; y [3] = 0; end
            2'b10: begin y [0] = 0; y [1] = 0; y [2] = I; y [3] = 0; end
            2'b11: begin y [0] = 0; y [1] = 0; y [2] = 0; y [3] = I; end
        endcase
    end
endmodule


```

### Output

 

### Design of 1:8 Demultiplexer

Input	Select lines			Output lines							
I	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
I	0	0	0	I	0	0	0	0	0	0	0
I	0	0	1	0	I	0	0	0	0	0	0
I	0	1	0	0	0	I	0	0	0	0	0
I	0	1	1	0	0	0	I	0	0	0	0
I	1	0	0	0	0	0	0	I	0	0	0
I	1	0	1	0	0	0	0	0	I	0	0
I	1	1	0	0	0	0	0	0	0	I	0
I	1	1	1	0	0	0	0	0	0	0	I

 


### Verilog code

```

module de_mux_1_8 (I, sel, y);
    input I;
    input [2:0] sel;
    output reg [7:0] y;
    always@(sel,I)
        case (sel)
            3'b000:begin y[0] = I; y[1] = 0; y[2] = 0; y[3] = 0; y[4] = 0; y[5] = 0; y[6] = 0; y[7] = 0;end
            3'b001:begin y[0] = 0; y[1] = I; y[2] = 0; y[3] = 0; y[4] = 0; y[5] = 0; y[6] = 0; y[7] = 0;end
            3'b010:begin y[0] = 0; y[1] = 0; y[2] = I; y[3] = 0; y[4] = 0; y[5] = 0; y[6] = 0; y[7] = 0;end
            3'b011:begin y[0] = 0; y[1] = 0; y[2] = 0; y[3] = I; y[4] = 0; y[5] = 0; y[6] = 0; y[7] = 0;end
            3'b100:begin y[0] = 0; y[1] = 0; y[2] = 0; y[3] = 0; y[4] = I; y[5] = 0; y[6] = 0; y[7] = 0;end
            3'b101:begin y[0] = 0; y[1] = 0; y[2] = 0; y[3] = 0; y[4] = 0; y[5] = I; y[6] = 0; y[7] = 0;end
            3'b110:begin y[0] = 0; y[1] = 0; y[2] = 0; y[3] = 0; y[4] = 0; y[5] = 0; y[6] = I; y[7] = 0;end
            3'b111:begin y[0] = 0; y[1] = 0; y[2] = 0; y[3] = 0; y[4] = 0; y[5] = 0; y[6] = 0; y[7] = I;end
            default: y = 8'bxxxxxxx;
        endcase
endmodule

```


### Output

 

The truth table of different types of de-mux 2:1, 4:1 and 8:1 are verified and simulated.

## 8. Design Verilog program for implementing various types of Flip-Flops such as SR, JK, and D.

### Design of SR Flip Flop

 

S	R	$Q_{n+1}$
0	0	$Q_n$ (No Change)
0	1	0
1	0	1
1	1	x


### Verilog Code

```


module sr(input clk, rst_n, input s,r, output reg q, output q_bar);
//always@(posedge clk or negedge rst_n) // for asynchronous reset
always@(posedge clk) begin // for synchronous reset
    if(!rst_n) q <= 0;
    else begin
        case({s,r})
            2'b00: q <= q; // No change
            2'b01: q <= 1'b0; // reset
            2'b10: q <= 1'b1; // set
            2'b11: q <= 1'bx; // Invalid inputs
        endcase
    end
end
assign q_bar = ~q;
endmodule

```

### Output

 

## Design of JK Flip Flop

 

J	K	$Q_{n+1}$
0	0	$Q_n$ (No Change)
0	1	0
1	0	1
1	1	$\overline{Q_n}$ (Toggles)

### Verilog code

```


module jk( input j, input k, input clk, output reg q);
always @ (posedge clk)

    case ({j,k})
        2'b00 : q <= q;
        2'b01 : q <= 0;
        2'b10 : q <= 1;
        2'b11 : q <= ~q;
    endcase

endmodule


```

### Output

 



## Design of D- Flipflop

 

## Verilog code:

```

module dd (
    input clk, rst_n, input d,
    output reg q
);
always@(posedge clk or negedge rst_n)
begin
    if(!rst_n) q <= 0;
    else q <= d;
end
endmodule

```

## Output

